

THE 'WINTON' Stereo Amplifier

Part 1

* E.A.RULE

The Winton amplifier has been designed primarily for the home constructor who would like a high fidelity amplifier equal to the best commercial design available, but at a price that enables it to be built within a sensible domestic budget, the total outlay being in the region of £110 for the complete project.

All the components are available and no special test equipment is needed for testing or setting up. The amplifier uses the very latest techniques and is capable of a standard of performance at least equal to the best commercial designs available with similar power ratings. In some aspects of its design it will outperform other amplifiers costing very much more.

Power f.e.t.s are used in the output stage and allow a wider power-bandwidth response with lower distortion than could be obtained if conventional bipolar output transistors were used. In the control unit section, bi-f.e.t. op.amps are used. These have an improved slew rate over the more common types, as well as much lower distortion. In the disc (magnetic) pre-amplifier, a three stage circuit using ultra low noise transistors enables noise figures of -68dB *unweighted* relative to 50W output to be obtained, with distortion so low that the input (normally 3mV) has to be increased to 140mV (+33dB) before the distortion even reaches 0.1%. A full circuit description will be given later.

On the front panel the Winton amplifier has controls for Volume, Balance, Bass, Treble and push buttons for selecting, Disc, Tuner, AUX 1, AUX 2, Tape monitor, Mono, h.f. and l.f. filters. Plus switches for mains on/off and loudspeaker or phones.

The headphone socket is also mounted on the front panel. DIN sockets are fitted on the rear panel for all inputs, terminals for the loudspeaker connections, an earth terminal, and fuse for the mains and each loudspeaker output. The heat sinks for the power f.e.t.s are also mounted on the rear panel.


Power f.e.t.s

Until recently bipolar transistors have been used in almost every Hi-Fi available (the exceptions using valves). Bipolar transistors require a wide area of Safe Operation to achieve reliability and a large gain-bandwidth product so that large amounts of negative feedback can be used at the higher audio frequencies to reduce the distortion. They also have a positive temperature coefficient which means that any increase in transistor temperature causes an increase in transistor collector current which causes the temperature to increase further, and so on requiring careful design to avoid thermal runaway. Also, as bipolar transistors are minority carrier devices, they suffer from storage effects at high frequencies which can cause a most objectionable distortion, which may well account for the so called "transistor sound".



In the light of all these problems a considerable amount of money and research has gone into looking for a better device. One result of this has been the power f.e.t.s developed by Hitachi Ltd., of Tokyo, Japan. Some advantages over conventional transistors are:

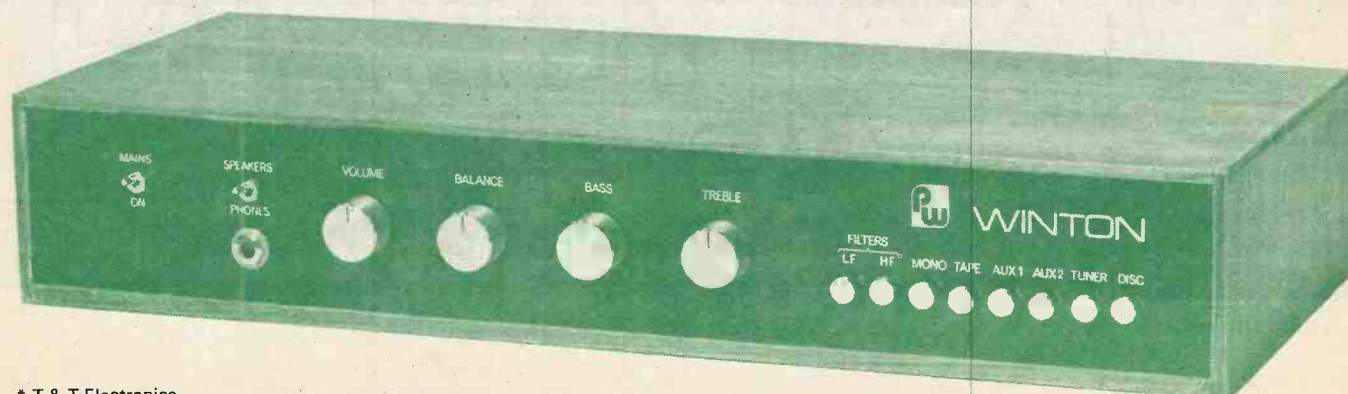- 1) Good frequency response because of fast carrier speed.
- 2) No storage effect.
- 3) Negative temperature coefficients, so no risk of thermal runaway.
- 4) No secondary breakdown.
- 5) High input impedance and high gain.

The Winton amplifier uses a complementary pair of Hitachi power f.e.t.s Type 2SJ48 (*p*-channel) and 2SK133 (*n*-channel). These devices have a maximum dissipation rating of 100W each, so when used in an amplifier of 50W output, each device is only dissipating about 25W, or just ticking over! In fact combined with a 120V drain to source breakdown voltage and a drain current of 7A they are almost indestructible when used in the Winton, which



* T & T Electronics

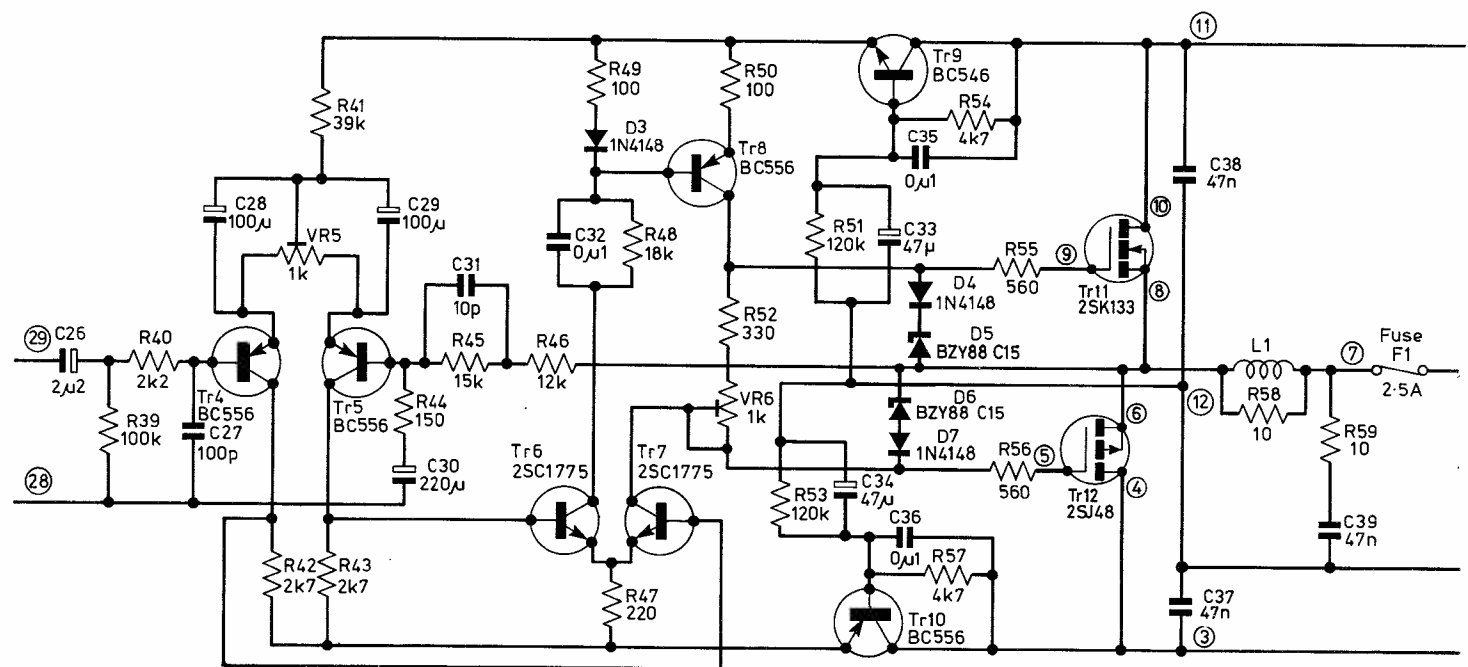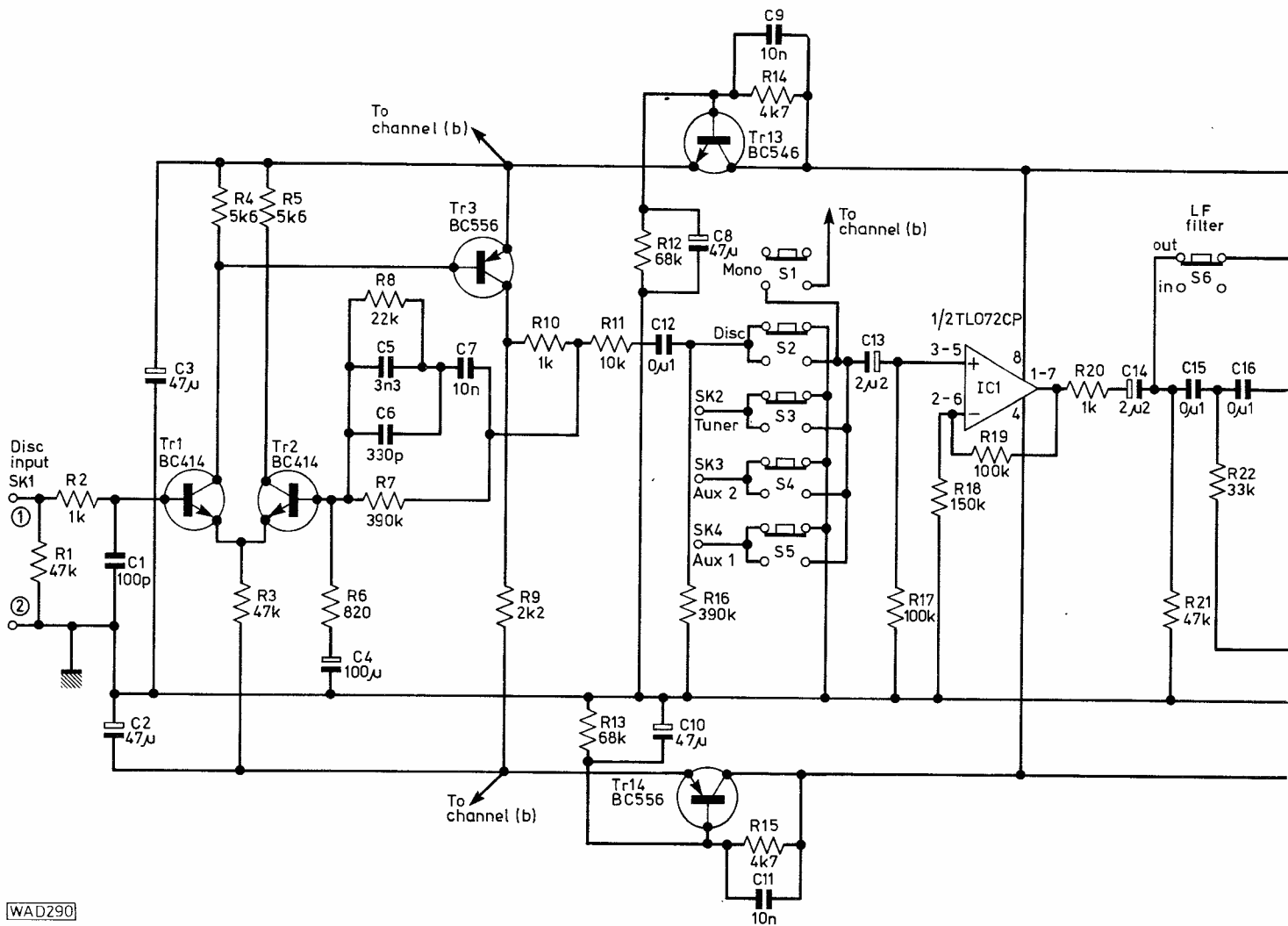

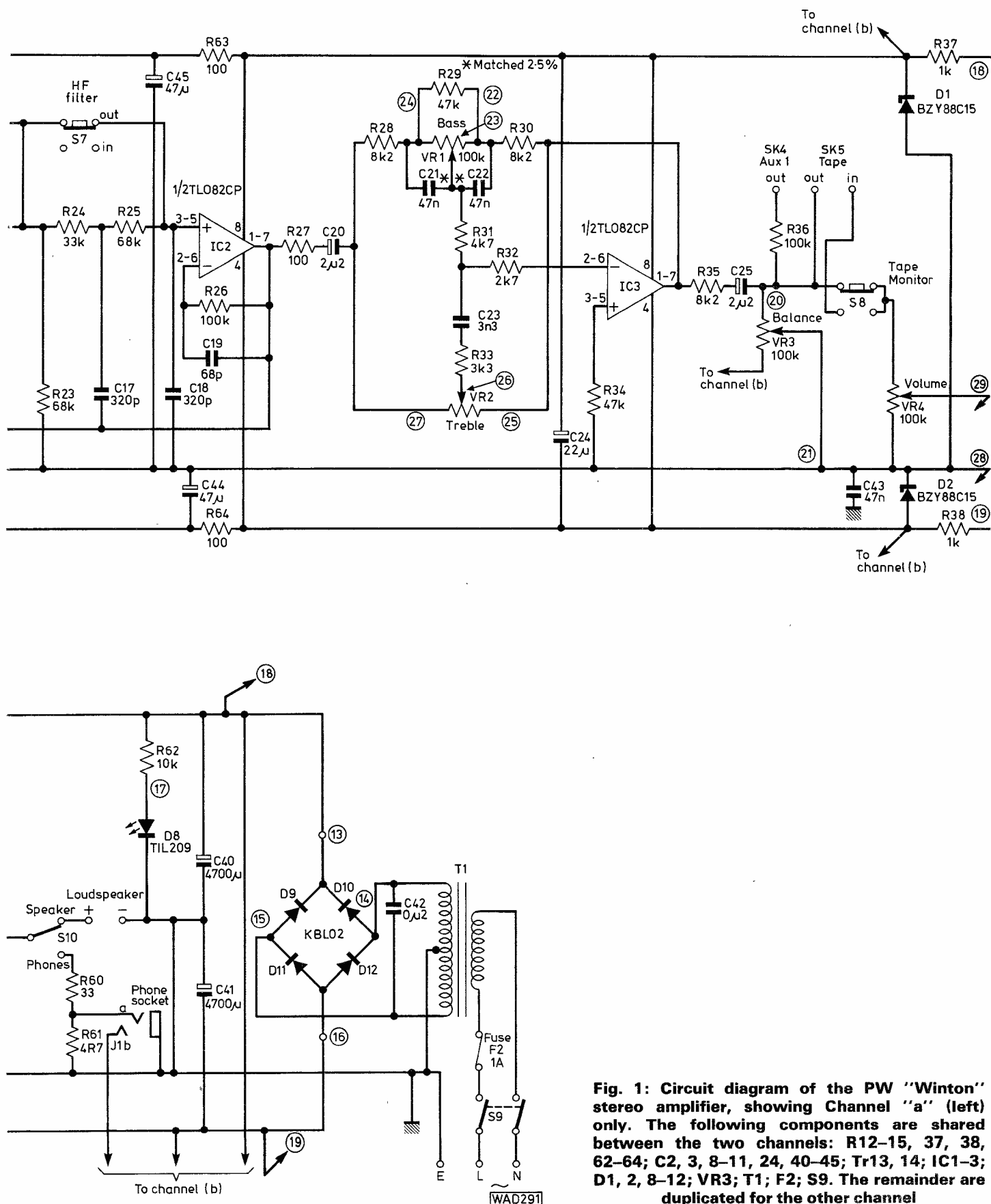


Fig. 1: Circuit diagram of the PW "Winton" stereo amplifier, showing Channel "a" (left) only. The following components are shared between the two channels: R12-15, 37, 38, 62-64; C2, 3, 8-11, 24, 40-45; Tr13, 14; IC1-3; D1, 2, 8-12; VR3; T1; F2; S9. The remainder are duplicated for the other channel

★ specification

Power Output

Continuous sine wave power, both channels driven
50 + 50W into 8Ω

Power Bandwidth (power amp. only)

−1dB 15Hz–100kHz

Frequency Response (power amp. only)

−0.5dB 10Hz–40kHz

−3dB 5Hz–150kHz

Harmonic Distortion (50 + 50W)

1kHz 0.013%

10kHz 0.015%

20kHz 0.018%

100Hz 0.011%

20Hz 0.019%

No significant increase at lower powers

Intermodulation Distortion (28V pk into 8Ω)

$f_1 = 15\text{kHz}$ $2f_1 - f_2$ 0.005%

$f_2 = 16\text{kHz}$ $2f_2 - f_1$ 0.004%

$f_2 - f_1$ 0.003%

Damping Factor

20Hz–1kHz 80

20kHz 20

Rise Time (power amp. only) 2μs

Slew Rate (power amp. only) 26V/μs

Stability – Unconditional

Sensitivity for 50W

Disc 3mV

Tuner 100mV

AUX 100mV

Tape 100mV

Input Impedance

Disc 47kΩ

Tuner 100kΩ

AUX 100kΩ

Tape 100kΩ

Maximum Input for 0.1% t.h.d.

Disc 140mV

Tuner 4V

AUX 4V


Frequency Response ±0.5dB

Disc RIAA


Tuner 20Hz–20kHz

AUX 20Hz–20kHz

Tape 10Hz–40kHz

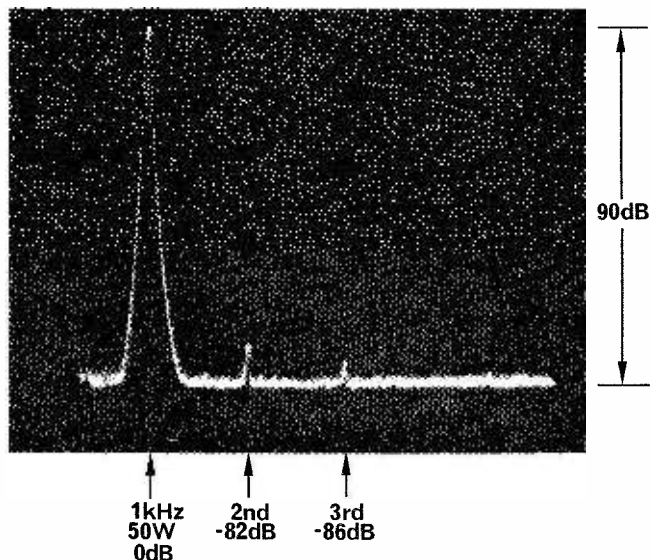


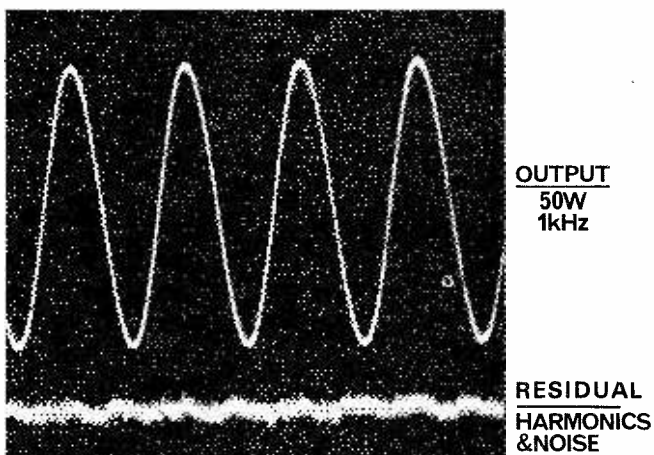Plot of Harmonic Distortion components generated when handling a 1kHz signal dissipating 50W in an 8Ω load. The 2nd harmonic is at −82dB and the 3rd harmonic −86dB relative to the fundamental



The upper trace shows the PW "Winton" output when handling a 1kHz signal dissipating 50W in an 8Ω load. Note the complete absence of crossover distortion

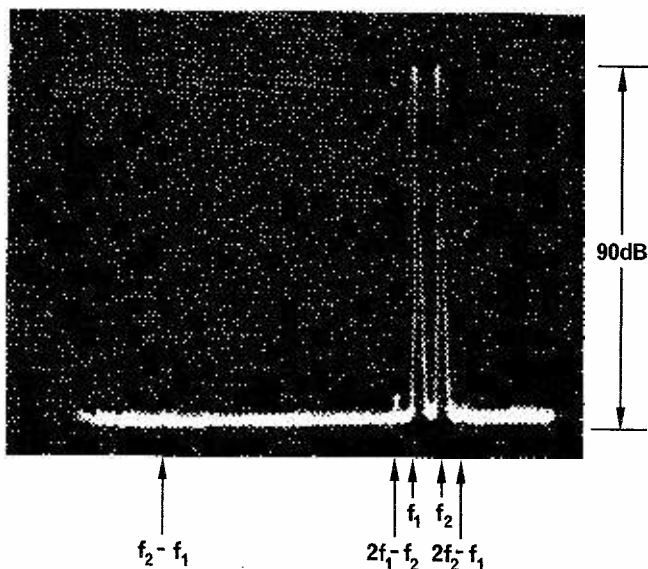The lower trace shows the residual harmonic content of the above signal, after the fundamental had been removed by the distortion meter filter. The total harmonic distortion is about −78dB, but is masked by noise



Plot of Intermodulation Distortion components generated when driven to full power into an 8Ω load by two equal-amplitude signals, $f_1 = 15\text{kHz}$, $f_2 = 16\text{kHz}$. Component $2f_1 - f_2$ is at -86dB , $2f_2 - f_1$ at -88dB , and $f_2 - f_1$ estimated at about -90dB

This test, using these frequencies, is very critical of the power-bandwidth capability of an amplifier, and is seldom given in specifications due to the generally poor figures obtained

Hum & Noise

Unweighted with reference to rated sensitivity*

Disc -70dB

Tuner -75dB

AUX -75dB

Tape -75dB

Hum & Noise

Disc input with reference to 10mV input

Unweighted 80.5dB

Cross Talk -48dB**

Tape Output 100mV

AUX 1 100mV via 100k Ω

* See comments regarding specifications.

** Important to note that cross talk residual is clean, i.e., does not introduce distortion into the other channel—a common failing in many amplifiers and seldom mentioned.

Tone Controls

Bass $\pm 10\text{dB}$ at 100Hz

Treble $\pm 10\text{dB}$ at 10kHz

Balance Control

$+0.5\text{dB}$ to zero, each channel

Channel Matching 0.5dB

Filters

l.f. -3dB 50Hz 12dB/Octave

h.f. -3dB 5kHz 12dB/Octave

Subsonic, disc only, non-switchable

(IEC 65) -3dB 20Hz

-8dB 10Hz

-17dB 5Hz

Ultrasonic, all inputs except tape, non-switchable

-3dB 60kHz

-7dB 100kHz

Before making any measurements, the amplifier was pre-conditioned for 1 hour at 30% full power with both channels driven. Measurements were made after a further 5 minutes at full power.

Unless otherwise stated, the volume control was at maximum, tone controls at centre and filters switched out.

The stability tests were made using various combinations of loads with capacitors up to $2\mu\text{F}$ and also with capacitors up to $2\mu\text{F}$ without additional load. Square wave signals were used over a frequency range of 20Hz to 20kHz.

The figures given are those obtained on the prototype amplifier.

Test Equipment

Hewlett Packard HP3580 spectrum analyser; Kron-Hite 4100 low distortion oscillator; Sound Technology 1700B distortion analyser, power output meter and low distortion oscillator; Telequipment D83 oscilloscope; Polaroid oscilloscope camera.

This equipment was kindly made available by Armstrong Audio Ltd., at their research laboratory.

General Comment

Be very careful when comparing specifications of other amplifiers with the Winton. Many other published specifications use a weighted signal to noise figure. This would allow an extra 10dB or so to be added to their figures and tends to favour the poorer quality amplifiers at the expense of the really good amplifiers.

means that the circuit can be kept simple as no protection circuits are required, eliminating another source of distortion.

The Bi-f.e.t. Op.amps

The use of the Texas bi-f.e.t.s in the control unit section offers a number of advantages over the more usual 741 type of op.amp. The main ones being:

- 1) Wider bandwidth. 3MHz typical.
- 2) High slew rate 13V/ μ s.
- 3) Low distortion 0.01%.
- 4) High input impedance j.f.e.t. input stage.
- 5) Low noise 18nV/Hz (TL072CP).
- 6) 80dB supply ripple rejection.

When used in low or unity gain circuits using large amounts of negative feedback the noise and distortion from the device is almost unmeasurable. The Winton amplifier has a basic sensitivity at the AUX inputs of 100mV and this has to be increased to 4V before the distortion reaches 0.1%. At any normally used input level the distortion is below the noise and completely inaudible.

Circuit Description

Both channels are identical and are pre-fixed "a" for left and "b" for right. Only the "a" channel will be described. See Fig. 1.

The Disc Pre-Amplifier

The input from a magnetic cartridge is fed into the base of Tr1, a low noise BC414 via the input load R1, 47k Ω , and an r.f. filter R2 C1. The transistor Tr1 forms one half of a differential input pair. Operating at a low current, approximately 100 μ A each half, ensures the minimum amount of noise.

The output from Tr1 is coupled directly to Tr3 a BC556. This in turn is coupled to a subsonic filter (as recommended by IEC65) consisting of C12, R16 and R17. This subsonic filter has its -3dB point at 20Hz, Fig. 2. This response, coupled with the normal RIAA response provides a 12dB/octave filter at subsonic frequencies and prevents intermodulation at low frequencies caused by warped records, etc., from being produced and affecting the overall sound quality. The RIAA negative feedback equalising circuit consists of R7, R8, C5, C7 and is connected between the output of Tr3 and the base of Tr2.

In order to ensure further the low noise factor in the disc amplifier, electronic decoupling is used, Tr13 (BC546) Tr14 (BC556) in each supply rail to remove any ripple or noise from the power supply. This supply has already been decoupled and stabilised by the Zener diodes, D1, D2.

The output from the disc pre-amplifier then goes to the selector switches S 1-5.

Control and Filter Section

From the selector switches S 1-5, each channel goes to one half of IC1 a bi-f.e.t. op.amp, Type TL072CP. This is used as a low noise buffer amplifier (with 4dB of gain) to provide a high impedance input, and a low impedance output suitable for driving the next stage, which also uses a bi-f.e.t. op.amp, Type TL082CP. This is used as an active high- (C15, C16, R22, R23) and low- (C17, C18, R24, R25) pass filter. Operating at unity gain, the filter is designed to provide a 12dB/octave cut-off with the -3dB points at 50Hz and 5kHz respectively, Fig 3. A slope of 12dB/octave is considered to be optimum for Hi-Fi use as a steeper slope could introduce ringing on transients, which would sound most objectionable.

The tone controls follow the filters, again using a bi-f.e.t. op.amp, Type TL082CP, and the circuit is a Baxandall negative feedback type.

This type of tone control circuit keeps distortion and noise to a much lower level than the passive type and also provides frequency response contours more acceptable to the ear, Fig. 4.

The amount of bass and treble boost and cut has been restricted to around + or - 10dB at 100Hz and 10kHz. Although it is possible to obtain up to 20dB boost and cut at these frequencies by removing R29 and reducing R33, extreme amounts of boost or cut are considered by the author to be bad design, as in practice large amounts can rarely be used. For example, suppose we have a signal requiring +10dB at 100Hz, with our circuit we can obtain this with only an extra dB or so at lower frequencies. If the unrestricted circuit was used, 10dB of boost at 100Hz would also produce 20dB of boost at 20Hz, as the response would continue to rise as shown in Fig. 4. The effect of this would be to increase all the rumble and other low frequencies a further 10dB over the required level at 100Hz. This would be in effect asking the amplifier for a considerable increase of power at low frequencies and as it cannot provide this, severe distortion would result. Note:

10dB of boost equals a voltage ratio of 3.16:1.

If our amplifier is already producing 50W into 8 Ω , i.e., 20V, then $20V \times 3.16 = 63.2V$, power = $V^2 \div R = 3994 \div 8 = 499.28$ watts!!

Even with the amount of boost restricted to + 10dB, if the bass control is at maximum and the amplifier is just reaching maximum power (50W) at say 20Hz then the maximum power at 1kHz must be limited to 5W (assuming a flat frequency response of the input signal). In practice, the tone controls are normally used to make up for the deficiency in the incoming signals, i.e., to restore the signal to an overall "flat" response, so the power restriction normally won't apply.

The output from the tone control circuit then passes to the balance control and the tape monitor switch S8. This switch selects either the output from the control unit section or the output from a tape recorder (connected to the tape socket) and feeds the signal via the volume control to the power amplifier. A tape output signal is permanently connected from the control unit output to both the tape socket and via 100k Ω resistors to the AUX 1 socket. This arrangement allows the use of either or both reel to reel and cassette recorders with the Winton. When using a reel to reel or cassette recorder fitted with a monitor head (plugged into the "tape" socket) tape monitoring can be achieved by simply pressing the "tape" button.

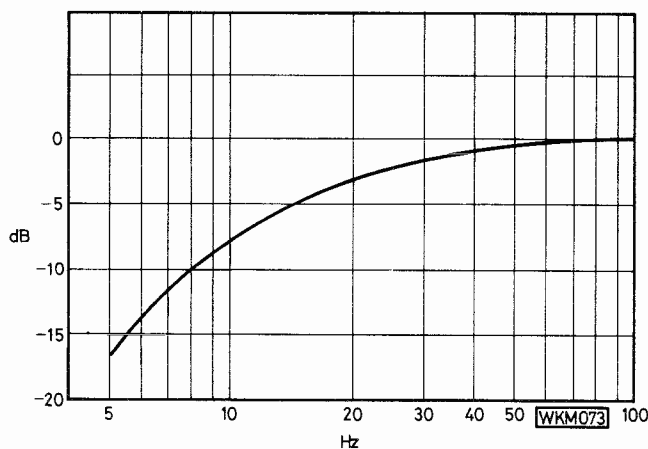


Fig. 2: Disc input — Subsonic filter response

Fig. 3: Frequency response of l.f. and h.f. filters

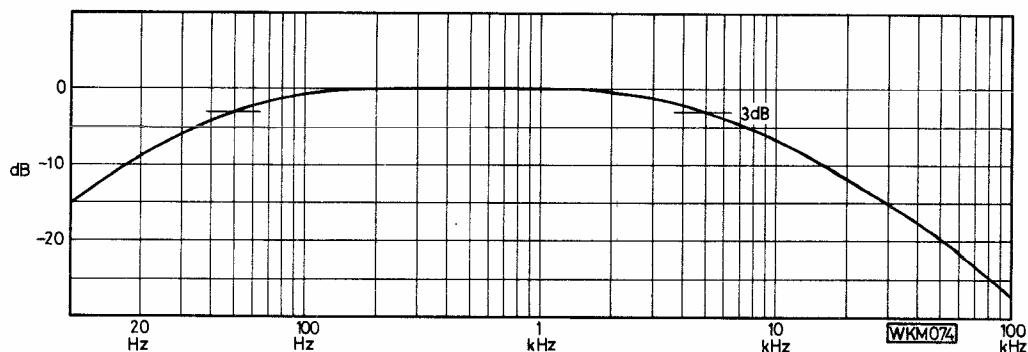


Fig. 4: Frequency response range of Bass and Treble controls


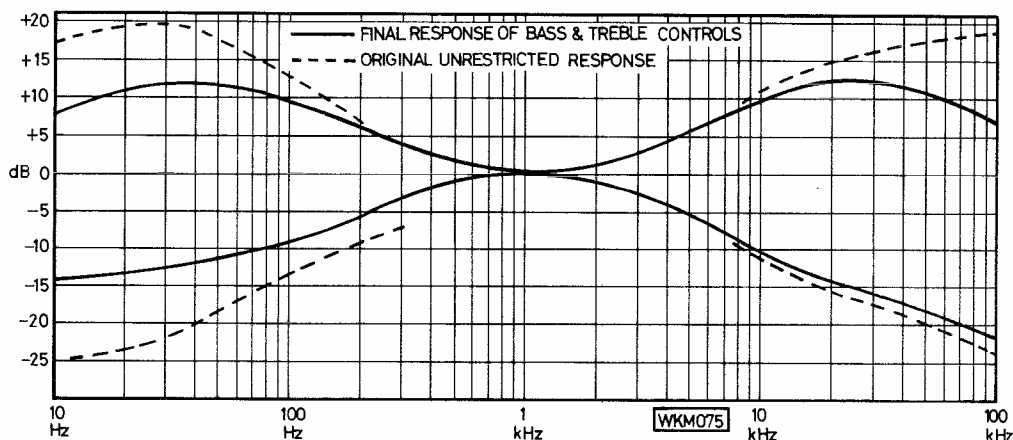


Fig. 5: Cross-talk between the two channels, for Disc and Auxiliary inputs

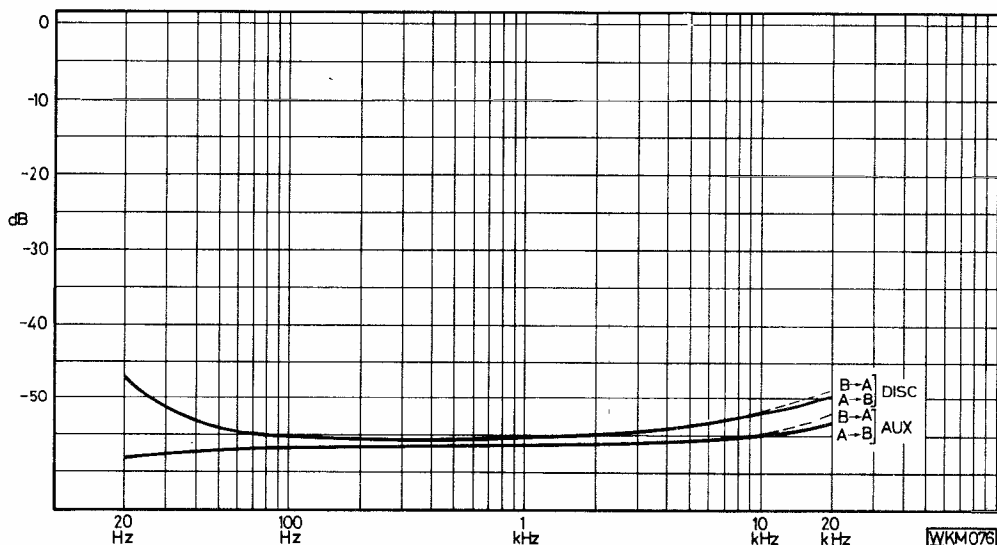

Power Amplifier

The circuit used for the power amplifier is based on a design produced by Hitachi for their power m.o.s.f.e.t.s. The original circuit has been modified by the author to suit the requirements of the Winton and electronic decoupling added to further improve the overall specification.

The signal from the volume control, VR4 is fed via an r.f. filter R40, C27 to the base of Tr4. This is one half of a differential pair Tr4, Tr5 using low noise transistors Type BC556. These in turn drive a second differential pair, Tr6, Tr7, Type 2SC1775, which has an active collector load (current mirror formed by Tr8 and D3), to maintain the pushpull action. The power m.o.s.f.e.t.s Tr11, Tr12 are driven directly from the second differential pair. As the

inherent distortion of the amplifier is very low, only 45dB of negative feedback is used, this is fed from the output, back to the base of Tr5 via R46, R45, C31. The use of less feedback means that, at the overload point, the onset of distortion is less severe than would be the case with amplifiers using considerably more negative feedback. Diodes D4, D7 and Zeners D5, D6 form an overdrive protection circuit to prevent the gates of the m.o.s.f.e.t.s from receiving excessive drive voltages in the event of a fault condition.

Due to the excellent high frequency response of the amplifier only minimal feedback phase correction is required via C31, R45, and L1, R58, R59, C39. The amplifier is unconditionally stable.

As mentioned earlier, electronic decoupling has been included in each power amplifier to reduce the power

★ components

Resistors

5% 0.25W

100Ω	8	R27, 49, 50, 63, 64
150Ω	2	R44
220Ω	2	R47
330Ω	2	R52
560Ω	4	R55, 56
820Ω	2	R6
1kΩ	6	R2, 10, 20
2.2kΩ	4	R9, 40
2.7kΩ	6	R32, 42, 43
3.3kΩ	2	R33
4.7kΩ	8	R14, 15, 31, 54, 57
5.6kΩ	4	R4, 5
8.2kΩ	6	R28, 30, 35
10kΩ	2	R11
12kΩ	2	R46
15kΩ	2	R45
18kΩ	2	R48
22kΩ	2	R8
33kΩ	4	R22, 24
39kΩ	2	R41
47kΩ	10	R1, 3, 21, 29, 34
68kΩ	6	R12, 13, 23, 25
100kΩ	10	R17, 19, 26, 36, 39
120kΩ	4	R51, 53
150kΩ	2	R18
390kΩ	4	R7, 16

5% 0.5W

10Ω	2	R59
10kΩ	1	R62

5% 1W

10Ω	2	R58
4.7Ω	2	R61
1kΩ	2	R37, 38

7W wirewound

33Ω	2	R60
-----	---	-----

Potentiometers

100kΩ + 100kΩ lin.	2	VR1, 2
100kΩ + 100kΩ log.	1	VR4
100kΩ lin.	1	VR3

Min. Preset horizontal mounting

1kΩ	4	VR5, 6
-----	---	--------

Switches

Min. toggle d.p.d.t.	2	S9, 10
Push button unit 8 keys	1	S1 to 8 (T & T Electronics)

Capacitors

Electrolytic

2.2μF 63V	10	C13, 14, 20, 25, 26
22μF 63V	1	C24
47μF 63V	10	C2, 3, 8, 10, 33, 34, 44, 45
100μF 16V	6	C4, 28, 29
220μF 16V	2	C30
4700μF 63V	2	C40, 41 (Note: 7A ripple rating)

Polystyrene

10pF	2	C31
60pF	2	C19
100pF	4	C1, 27
320pF	4	C17, 18
330pF	2	C6
3.3nF	4	C5, 23
10nF	2	C7

Polyester

0.2μF	1	C42
0.1μF	12	C12, 15, 16, 32, 35, 36
47nF	7	C37, 38, 39, 43
47nF	4	C21, 22 (Note: matched 2-5%)
10nF	2	C9, 11

Semiconductors

Diodes

TIL209	1	D8
BZY88C15	6	D1, 2, 5, 6
1N4148	6	D3, 4, 7
KBL-02	1	D9-12

Transistors


BC414	4	Tr1, 2
BC556B	11	Tr3, 4, 5, 8, 10, 14
BC546B	3	Tr9, 13
2SC1775E	4	Tr6, 7
2SK133	2	Tr11
2SJ48	2	Tr12

Integrated Circuits

TL072CP	1	IC1
TL082CP	2	IC2, 3

Miscellaneous

PCB Winton (T & T Electronics), Mains Transformer, Belcleps 6854/3 (T & T Electronics), Chassis and front panel, Winton (T & T Electronics), Case Winton (T & T Electronics), Pins, RS 433-630 (47); Fuse holder, RS 412-879 (3); Fuse 2.5A Quick Blow (2); Fuse, 1A Slow-Blow (1); Pillars, RS 543-737 (5); Cable Ties, RS 543-349 (8); Cable Ties, RS 543-428 (6); 4mm Terminals, Black (1), Blue (2), Red (2); DIN Socket 5-way 180° (5); Jack Socket, RS 478-015 (1).

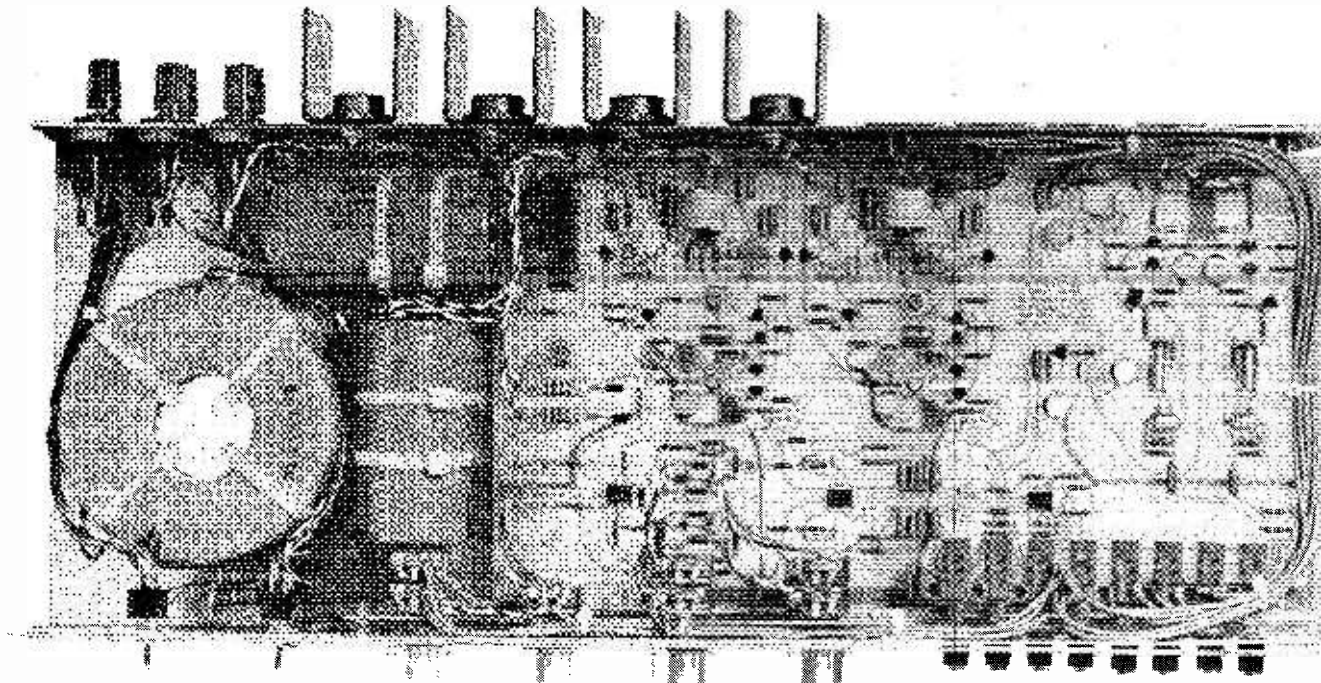

Internal view of the PW "Winton" amplifier. Here, we show the final version using a printed circuit board. The model illustrated on our front cover is the prototype, which was constructed on perforated board with hard wiring

supply noise and ripple voltage, as well as improving the cross-talk (Fig. 5) between channels. Transistors Tr9, BC546 and Tr10, BC556 are used for the decoupling circuit.

Provision is made to adjust the d.c. offset at the output to zero. By adjusting VR5, the current through the differential input stage can be adjusted to compensate for the slight gain variation in each half of the differential pairs. It is very important that the output from the amplifier does not contain any d.c. voltage, as this would cause the loudspeaker cone to take up a position away from its centre which in turn would cause distortion because of the resulting non-linear cone movement.

Power Supply

By no means least important, the power supply of the Winton has been subjected to the same standard of design as the rest of the circuits, although on the surface it may look simple.

In a high fidelity amplifier the power supply can either turn a good amplifier into a top quality model or into a not so good one. There are two main reasons for this:

- 1) The regulation of the supply volts must enable the amplifier to reach its full power potential under the worst possible signal conditions. At the same time, it must not let the voltage rise to dangerous levels under quiescent conditions.
- 2) The external magnetic field from the transformer must not inject any hum into the amplifier circuits, particularly the disc amplifier.

To enable the full performance that the Winton is capable of to be achieved, it was decided to use a toroidal type of transformer. The design and development of this special low-field transformer was carried out by Belclere Ltd., and this transformer is now available from T & T Electronics.

The output from the transformer goes to a bridge rectifier and then to the two 4700 μ F capacitors C40, C41. These, and the electronic decoupling circuits used in the

power amplifiers, coupled with the Zener stabilised supply to the control unit and further electronic decoupling to the disc pre-amplifier, ensure that only about 0.001% of the total output from the Winton is noise from the power supply. Even on the disc input the total noise in the output from all sources combined is only about 0.04%.

Heat Sink Ratings

When designing an amplifier for domestic use, the design is almost always a compromise between all the various requirements. In the case of the Winton amplifier this applies to the size of the heat sink and mains transformer.

It is possible to make both of these components in such a way that the amplifier could deliver 50 + 50W continuous power for hours on end without much temperature rise. The cost of doing this would be so high as to put the amplifier out of reach of most peoples' budget. On the other hand these components could be made down to a low price and the amplifier allowed to run very hot, which would lower the reliability.

In the design of the Winton the author has arranged that these two components will allow the power f.e.t.s and the transformer to run well inside their respective maximum rating under continuous drive conditions, although under these conditions both the heat sink and transformer will reach quite high temperatures and certainly be too hot to touch.

When used for its normal purpose, i.e., reproducing music, the temperature rise is very much less and after some hours of loud music will still be only moderately "Hot". The actual heat sink may reach 60°C under these conditions.

This compromise doesn't reduce the quality of the reproduced sound in any way, but it does avoid a severe pain in the wallet.

NEXT MONTH
Constructional details